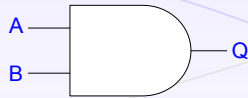


Logic Tables


09/03/2005

AND




A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

NAND

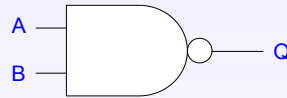


A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

OR

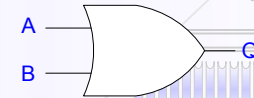

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

NOR

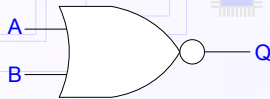


A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

XOR



A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

NOT

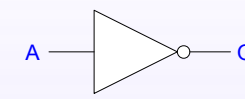

A	Q
0	1
1	0